

Overview

30 September 2019 11:32

Course Homepage

<https://intranet.ee.ic.ac.uk/t.clarke/ee2lab/>
<https://intranet.ee.ic.ac.uk/intranet/labweb/>
http://www.ee.ic.ac.uk/pcheung/teaching/E2_Experiment/

Timetable

Screen clipping taken: 30/09/2019 11:35

Aims:

The laboratory course aims to introduce you to best practice in experimental work, while supporting the lecture courses and giving practical exposure to real systems.

Learning Outcomes:

You will learn to use test equipment with accuracy and confidence, while deepening your understanding of the taught material by gaining practical insight and skills.

Syllabus:

Hardware experiments in Communications, Control, uP A/D & D/A. Software experiments in Signal processing & Communications (MATLAB).

From <http://intranet.ee.ic.ac.uk/electricalengineering/eecourses_t4/course_content.asp?c=EE2-ILAB&s=l2#start>

Declare all inputs/outputs in module, name the module the same as file name

Declare all the things in module as input/output, any variables declare as reg, and things you want constant declare as parameters. Parameters allow you to generalise your module blocks to be reused with a different specification, defparam can be used to override the parameter initialisation.

If enable is set, then count increments on the rising edge of clock. You do not need to reset count, as it will roll over to 0 when it increments past its bit width.

Changed BIT_SZ to 16 so that the counter now counts up to 16 not 8.

In the always block, added 'if reset == 0' to provide resetting functionality. This is synchronous, if it was in the sensitivity list as well as the clock it would be asynchronous.

In the top level function we edit the previous code by making the binary BCD by calling the new module bin2bcd_10

The 7 seg modules are called like before

We change the hex to 7seg file so that it only goes 0-9

Only the very first inputs, and final outputs are in the module list. All intermediary inputs/outputs of modules are labelled as wire.

Each module is called and the wires connect them together

KEY[0] is reset, and is inverted (using ~) before entering the counter module to meet the specifications required.

This is 4bit LFSR so repeats every $2^4-1 = 15$ cycles

This is the code for the X^7 LFSR

XOR gate makes a random sequence (repeating every $2^7 - 1$ cycles)

`{}` mean concatenation (what does this mean?)

To make the LFSR from X^4 to $1 + X + X^7$ we change what is XOR to the first and last registers, and then change the number of registers to 7

Output = high, Count until data in, at which point set output = low this produces a signal with high's based on b

Declares the I/O

Defines the I/O

Calls the pwm module

DAC_SCK

DAC_SDI

TP8

TP5

The signals are the same, so that shows that it doesn't matter whether we use pwm or the DAC, it gives the same result.

TP9

TP5

To attenuate by 0.5, it is dividing by 2, so shift right by 1.


FIFO can be used to implement constant delay

Part 1

06 December 2019 20:09

Part 1

Block diagram of the DE1-SOC board:

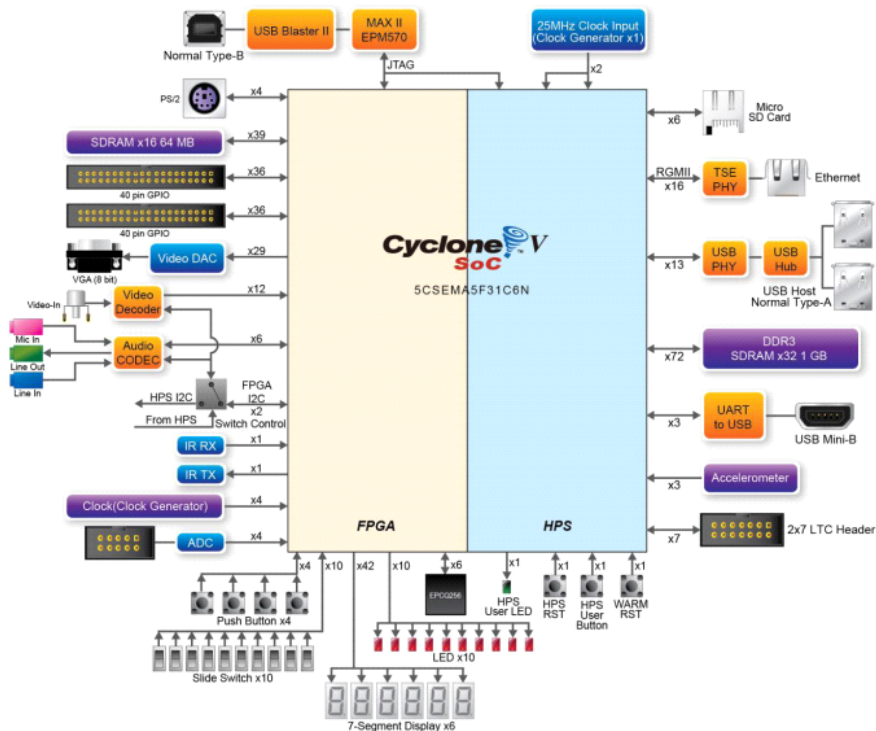


Ex1: Boolean equation for $out[4] = /in3*in0 + /in3*in2*/in1 + /in2*/in1*in0$

Using the graphic editor:

Clicking on the gate icon or workspace allows you to place gates, click on the gates legs and move the cursor to add wires.
Once schematic for a block section is finished create a symbol for it in create/update.
Create a top level file to indicate how the I/O of the chip should interact with your design.

To program FPGA:

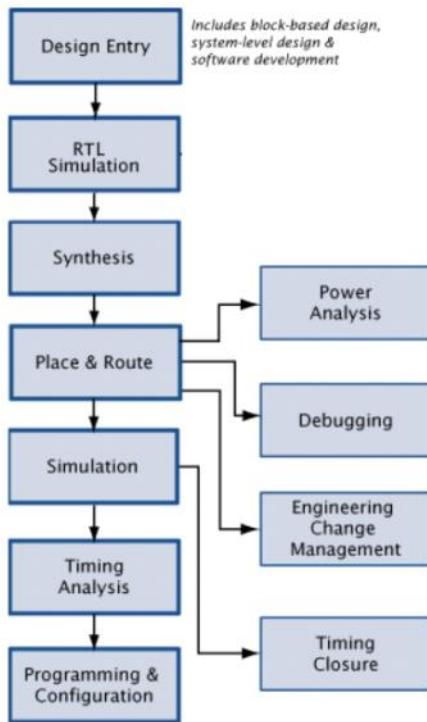1. Analysis and Elaboration
2. Compilation
3. Program the FPGA
 - a. tools -> programmer
 - b. Hardware setup -> DE-SOC
 - c. Auto detect -> 5SC... -> delete SOC -> add files -> output files -> select file.



Screen clipping taken: 04/12/2019 15:16

Analysis & Synthesis optimises the design considering the specific logic. It checks for logical completeness and checks for syntax errors (spelling, incorrect port names etc). It optimises the design for the specific device used. It uses algorithms to minimise gate count and redundant logic, as well as use the device architecture as efficiently as possible. It creates state assignments for state machines and reduces resources used. It then maps combinational resources to individual cell-sized logic units. Builds a database that integrates all the design files in the design. Creates a register level model of design for RTL simulation.

Analyse current file: To check current file for syntax and semantics errors.

Analysis and elaboration: Partially compiles the current design.

Pin assignments can be done inside the pin planner, or in the .qsf file.

Set_instance_assignment -name //SomeName// "3.3-V LVTTTL" -to HEX0[4]

Defines the voltage

Set_location_assignment //PIN NAME// -to HEX0[4]

Defines the pin location of HEX0[4] to pin name.

In order to compile we need to assign pins so that Quartus knows which signal to connect to which pin on FPGA.

Top level specification:

Can be the .bdf file or .v Verilog file.

Compilation generates a .sof file. It uses the Analysis & synthesis, Fitter, Assembler, Design Assistant and Timing Analyser to create a programming file (a file that programs the board).

The first experiment involved programming a 7 segment display decoder using schematic capture on Quartus. The following are timing analyser reports at different temperatures:

TimeQuest Timing Analyzer - H:/VERU/Part 1/Ex_1/my7seg - my7seg

Set Operating Conditions: Slow 1100mV 85C Model, Slow 1100mV 0C Model, Fast 1100mV 85C Model, Fast 1100mV 0C Model

Report: TimeQuest Timing Analyzer Summary, Advanced I/O Timing, Datasheet Report, Propagation Delay, Minimum Propagation Delay

Input Port	Output Port	RR	RF	FR	FF
1 SW[0]	HEX0[0]	8.469	8.618	8.981	9.138
2 SW[0]	HEX0[1]	8.669	9.017	9.181	9.583
3 SW[0]	HEX0[2]		8.896	9.197	
4 SW[0]	HEX0[3]	8.113	8.212	8.621	8.774
5 SW[0]	HEX0[4]	8.886			9.712
6 SW[0]	HEX0[5]	8.771			9.718
7 SW[0]	HEX0[6]	8.209	8.226	8.720	8.745
8 SW[1]	HEX0[0]	8.127	8.297	8.669	8.821
9 SW[1]	HEX0[1]	8.422	8.719	8.970	9.244
10 SW[1]	HEX0[2]	8.335			9.095
11 SW[1]	HEX0[3]	7.910	7.958	8.461	8.486
12 SW[1]	HEX0[4]		8.871	9.086	
13 SW[1]	HEX0[5]	8.530	8.861	9.079	9.387
14 SW[1]	HEX0[6]	7.867	7.905	8.409	8.429
15 SW[2]	HEX0[0]	8.669	8.893	9.202	9.479
16 SW[2]	HEX0[1]	9.144			9.960
17 SW[2]	HEX0[2]	8.889	9.177	9.422	9.783
18 SW[2]	HEX0[3]	8.585	8.610	9.118	9.151
19 SW[2]	HEX0[4]	9.086	9.467	9.619	10.053
20 SW[2]	HEX0[5]	9.246	9.554	9.779	10.095
21 SW[2]	HEX0[6]	8.409	8.501	8.942	9.087
22 SW[3]	HEX0[0]	8.277	8.486	8.746	8.905
23 SW[3]	HEX0[1]	8.572	8.917	9.106	9.448
24 SW[3]	HEX0[2]	8.505	8.780	8.975	9.196
25 SW[3]	HEX0[3]	8.012	8.108	8.626	8.639
26 SW[3]	HEX0[4]	9.965	9.169		
27 SW[3]	HEX0[5]	8.673	9.052	9.287	9.583
28 SW[3]	HEX0[6]	8.013	8.092	8.483	8.510

Propagation Delay: Reports longest delay in nanoseconds between the edges of a signal propagating from an input port to an output port. a. RR shows the longest delay measured from rising edge to rising edge b. RF shows the longest delay measured from rising edge to falling edge c. FR shows the longest delay measured from falling edge to rising edge d. FF shows the longest delay measured from falling edge to falling edge Note that, in the propagation delay the highest delay (Worst-Case) is important

The Rise and fall times seem to be generally longer at 85 degrees than 0 degrees because of more power wastage at higher temperatures.

Flow Summary	
Flow Status	Successful - Tue Nov 14 10:50:23 2017
Quartus Prime Version	16.0.0 Build 211 04/27/2016 SJ Standard Edition
Revision Name	my7seg
Top-level Entity Name	my7seg
Family	Cyclone V
Device	5CSEMA5F31C6
Timing Models	Final
Logic utilization (in ALMs)	4 / 32,070 (< 1 %)
Total registers	0
Total pins	11 / 457 (2 %)
Total virtual pins	0
Total block memory bits	0 / 4,065,280 (0 %)
Total DSP Blocks	0 / 87 (0 %)
Total HSSI RX PCSs	0
Total HSSI PMA RX Deserializers	0
Total HSSI TX PCSs	0
Total HSSI PMA TX Serializers	0
Total PLLs	0 / 6 (0 %)
Total DLLs	0 / 4 (0 %)

Here we can see only 11 pins and 4 ALUs are used due to optimisation that the software provides.

Exercise 2

In this experiment, we Verilog hardware description language to implement the 7 segment decoder.

Hex to 7 seg module

```
module hex_to_7seg (out,in);

    output [6:0] out; //low-active output
    input [3:0] in; //4-bit binary input

    reg [6:0] out;

    always @ (*)
        case (in)
            4'h0: out = 7'b1000000;
            4'h1: out = 7'b1111001;
            4'h2: out = 7'b0100100;
            4'h3: out = 7'b0110000;
            4'h4: out = 7'b0011001;
            4'h5: out = 7'b0010010;
            4'h6: out = 7'b0000010;
            4'h7: out = 7'b1111000;
            4'h8: out = 7'b0000000;
            4'h9: out = 7'b0011000;
            4'ha: out = 7'b0001000;
            4'hb: out = 7'b0000011;
            4'hc: out = 7'b1000110;
            4'hd: out = 7'b0100001;
            4'he: out = 7'b0000110;
            4'hf: out = 7'b0001110;

        endcase

    endmodule
```

Always @ (*) means any input variable used inside this block will be in the sensitivity list (i.e. this block will execute if any of them change). Reg is used to declare a variable that holds a value, and can be changed anytime in a simulation.

Top level module

```

module ex2_top (
    SW,
    HEX0
);

    input[3:0] SW;
    output[6:0] HEX0;

    hex_to_7seg    SEG0 (HEX0,SW);

endmodule

```

Using Verilog HDL was much less tedious and less prone to errors than using schematic capture.

Exercise 3

Top level module

```

module ex3_top(SW,HEX0,HEX1,HEX2);

    input [9:0] SW; //INPUT SWITCHES
    output [6:0] HEX0,HEX1,HEX2;


    hex_to_7seg    SEG0(HEX0,SW[3:0]);
    hex_to_7seg    SEG1(HEX1,SW[7:4]);
    hex_to_7seg    SEG2(HEX2,{2'b0,SW[9:8]});

endmodule

```

Here the {2'b0, SW[9:8]} means concatenation, so the result of this is number: 00XY
Where X = SW[9] and Y = SW[8]


Optional - Exercise 4

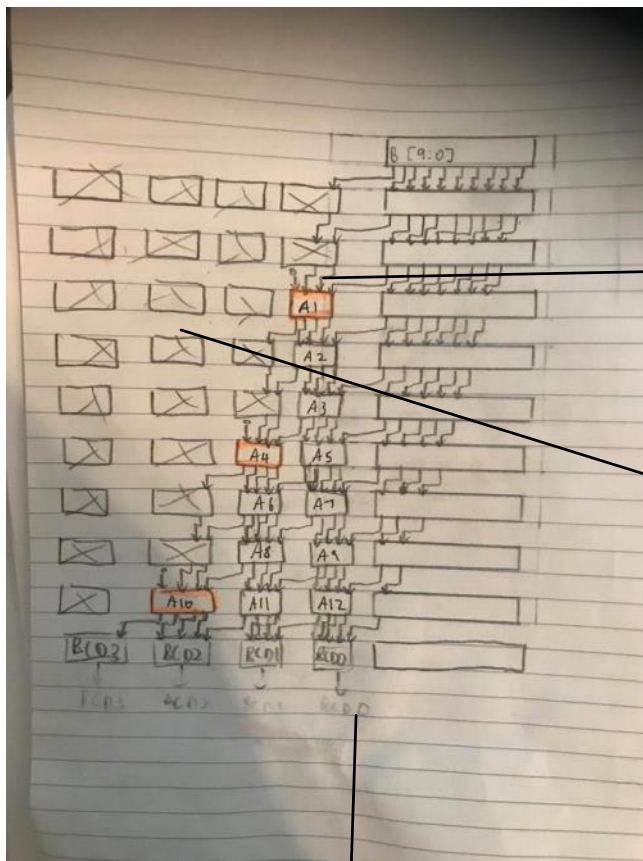


This exercise involved extending the theory for a 8 bit binary to BCD convertor into 10 bit. We followed the shift and add algorithm to come up the following mappings which we then coded as shown below.

At each orange box, a new 'wire' is created as a new bit would be required if the value inside adjust box is greater than 4.

 We only need to code adjust boxes where the value could be greater than 4- ignore the rest.



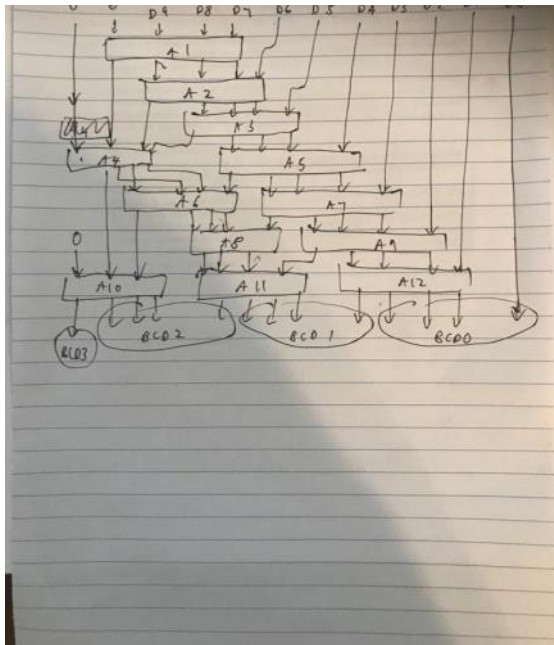

Top level module

```

module Ex_4_top (HEX0, HEX1, HEX2, HEX3, SW);
input [9:0] SW;
output [6:0] HEX0, HEX1, HEX2, HEX3 ;
wire [3:0] BCD0, BCD1, BCD2, BCD3;

bin2bcd_10 CONVERTER (SW, BCD0, BCD1, BCD2, BCD3);
hex_to_7seg SEG0 (HEX0, BCD0);
hex_to_7seg SEG1 (HEX1, BCD1);
hex_to_7seg SEG2 (HEX2, BCD2);
hex_to_7seg SEG3 (HEX3, BCD3);
endmodule

```

```

module bin2bcd_10 (B, BCD_0, BCD_1, BCD_2,BCD_3);

    input [9:0] B;        // binary input number
    output [3:0] BCD_0, BCD_1, BCD_2, BCD_3;    // BCD digit LSD to MSD

    wire [3:0] w1,w2,w3,w4,w5,w6,w7,w8,w9,w10,w11,w12;
    wire [3:0] a1,a2,a3,a4,a5,a6,a7,a8,a9,a10,a11,a12;

    // Instantiate a tree of add3-if-greater than or equal to 5 cells
    // ... input is w_n, and output is a_n
    add3_ge5 A1 (w1,a1);
    add3_ge5 A2 (w2,a2);
    add3_ge5 A3 (w3,a3);
    add3_ge5 A4 (w4,a4);
    add3_ge5 A5 (w5,a5);
    add3_ge5 A6 (w6,a6);
    add3_ge5 A7 (w7,a7);
    add3_ge5 A8 (w8,a8);
    add3_ge5 A9 (w9,a9);
    add3_ge5 A10 (w10,a10);
    add3_ge5 A11 (w11,a11);
    add3_ge5 A12 (w12,a12);

    // wire the tree of add3 modules together
    assign w1 = {1'b0, B[9:7]};    // wn is the input port to module An
    assign w2 = {a1[2:0], B[6]};
    assign w3 = {a2[2:0], B[5]};
    assign w4 = {1'b0, a1[3], a2[3], a3[3]};
    assign w5 = {a3[2:0], B[4]};
    assign w6 = {a4[2:0], a5[3]};
    assign w7 = {a5[2:0], B[3]};
    assign w8 = {a6[2:0], a7[3]};
    assign w9 = {a7[2:0], B[2]};
    assign w10 = {1'b0, a4[3], a6[3], a8[3]};
    assign w11 = {a8[2:0], a9[3]};
    assign w12 = {a9[2:0], B[1]};

    // connect up to four BCD digit outputs
    assign BCD_0 = {a12[2:0], B[0]};
    assign BCD_1 = {a11[2:0], a12[3]};
    assign BCD_2 = {a10[2:0], a11[3]};
    assign BCD_3 = a10[3];

endmodule

```

```

1 module hex_to_7seg (out, in);
2     output [6:0] out;
3     input [3:0] in;
4
5     reg [6:0] out;
6
7     always @ (*)
8     case (in)
9         4'h0: out = 7'b1000000;
10        4'h1: out = 7'b1111001;
11        4'h2: out = 7'b0100100;
12        4'h3: out = 7'b0110000;
13        4'h4: out = 7'b0011001;
14        4'h5: out = 7'b0010010;
15        4'h6: out = 7'b0000010;
16        4'h7: out = 7'b1111000;
17        4'h8: out = 7'b0000000;
18        4'h9: out = 7'b0011000;
19        4'ha: out = 7'b0001000;
20        4'hb: out = 7'b0000011;
21        4'hc: out = 7'b1000110;
22        4'hd: out = 7'b0100001;
23        4'he: out = 7'b0000110;
24        4'hf: out = 7'b0001110;
25    endcase
26 endmodule

```

```

1 module add3_ge5(iw,oA);
2
3     input [3:0] iw;
4     output reg [3:0] oA;
5
6     always @ (iw)
7     case (iw)
8         //***** input <5, pass to output unchanged *****
9         4'b0000: oA <= 4'b0000;
10        4'b0001: oA <= 4'b0001;
11        4'b0010: oA <= 4'b0010;
12        4'b0011: oA <= 4'b0011;
13        4'b0100: oA <= 4'b0100;
14
15        //***** input >=5, output = input + 3 *****
16        4'b0101: oA <= 4'b1000;
17        4'b0110: oA <= 4'b1001;
18        4'b0111: oA <= 4'b1010;
19        4'b1000: oA <= 4'b1011;
20        4'b1001: oA <= 4'b1100;
21        4'b1010: oA <= 4'b1101;
22        4'b1011: oA <= 4'b1110;
23        4'b1100: oA <= 4'b1111;
24        default: oA <= 4'b0000; // oA cannot be 13 or larger, else overflow
25    endcase
26 endmodule

```

This module implements the 10 bit binary to bcd conversion.

It assigns the values to in, and calls the add3shift module.

Then it assigns the BCD outputs.

Part 2

06 December 2019 20:09

Outcomes:

- Using Modelsim to verify correct function of your design and testbenches
- How to design different types of counters and timers
- Predict max operating clock frequency of circuit

Experiment 5

`timescale time_unit / time_precision : time_unit and precision take in arguments magnitude(1, 10 or 100) and unit time (s,ms, us, ns, ps, fs). Time precision must be <= time unit value. Time unit is the measurement of delays and simulation time, time precision is how delay values are rounded before being used. When a delay is given (e.g. #1) then it is multiplied with time_unit, and rounded by time_precision.

To set as top level entity = Project -> add as top level entity

8 bit counter module:

```
timescale 1ns / 100ps // unit time is 1ns, resolution 100ps
//----- Design Name: counter_8
//----- Function : an 8-bit synchronous counter with enable input
//-----

module counter_8 (
    clock, // clock input
    enable, // high enable counting
    count // count value
);
//----- Declare ports -----
parameter BIT_SZ = 8;
input clock;
input enable;
output [BIT_SZ-1:0] count;

// count needs to be declared as reg
reg [BIT_SZ-1:0] count;

//---- always initialise storage elements such as D-FF
initial count = 0;

//---- Main body of the module -----
always @ (posedge clock)
    if (enable == 1'b1)
        count <= count + 1'b1;
endmodule // end of module
```

Screen clipping taken: 04/12/2019 16:23

This counts up to the parameter BIT_SZ which can be adjusted for other sizes.

Blocking vs Non-blocking:

```
a = b; blocking
b = a;
// both a & b = b
```

Screen clipping taken: 09/12/2019 16:11

```
a <= b; Non-blocking
b <= a;
// swap a and b
```

Screen clipping taken: 09/12/2019 16:11

For non-blocking the statements are executed in parallel, for blocking they are executed sequentially.

Modelsim

You must tell Modelsim what to simulate by doing Simulate -> Start simulation, then work -> myFile.

Do files:

Allow you to write a testbench for your code, where you can single step through to find errors.



Output from Modelsim

Question answers:

- Predicted max frequencies for this circuit: 85C - 445.04MHz, 0C - 422.48MHz
- Input / Output ports and paths are unconstrained - the outputs/inputs to the circuit are not timing constrained - the inputs may change without any clock as they are not held (it cannot make a full time analysis as it doesn't know if the inputs may change).

Experiment 6:

Module counter_16

```

`timescale 1ns / 100ps           //unit time is 1ns, resolution is 100ps

//Design Name: counter_16
//Function: a 16-bit synchronous counter with enable input

module counter_16 (
    clock, //clock input
    enable, //high enable counting
    reset,
    count
);

//Declaring the ports:

    parameter BIT_SZ = 16;
    input clock;
    input enable;
    input reset;
    output [BIT_SZ-1:0] count;

// count needs to be declared as reg which can save values assigned to it

    reg [BIT_SZ-1:0] count;

//always initialise storage elements such as D-FF
    initial count = 0;

//MAIN BODY OF MODULE:

    always @ (posedge clock)
    begin
        if(enable == 1'b1)
            count <= count + 1'b1;
        if(reset == 1'b1)
            count <= 1'b0;
    end
endmodule

```

To convert the 8 bit counter to 16 bits, simply change the parameter BIT_SZ. To reset synchronously to the clock we add if(reset) inside the always block. If we wanted it to reset asynchronously we could put it in the sensitivity list.

Top level module:

```

module ex6_top(KEY,CLOCK_50,HEX0,HEX1,HEX2,HEX3,HEX4);

    input [1:0] KEY;
    wire [3:0] BCD0,BCD1,BCD2,BCD3,BCD4;
    input CLOCK_50;
    output [6:0] HEX0,HEX1,HEX2,HEX3,HEX4;
    wire [15:0] counter;

    counter_16 temp0(CLOCK_50,~KEY[0],~KEY[1],counter);

    bin2bcd_16 temp1(counter,BCD0,BCD1,BCD2,BCD3,BCD4);

    hex_to_7seg temp2(HEX0,BCD0);
    hex_to_7seg temp3(HEX1,BCD1);
    hex_to_7seg temp4(HEX2,BCD2);
    hex_to_7seg temp5(HEX3,BCD3);
    hex_to_7seg temp6(HEX4,BCD4);

endmodule

```

For the top level we just needed to call the counter, call the bin2bcd and call the hex to 7 seg modules. The keys were inverted to meet the specification using the bitwise inverter (~). It was more generic to invert them here than change the module.


To create a clock frequency:

- Make myName_top.sdc file
- Create_clock -name "myName" -period xs [get_ports {myName}]

Timing analysis results:

Resource	Usage
Estimate of Logic utilization (ALUTs needed)	92
Combinational ALUT usage for logic	166
-- 7 input functions	0
-- 6 input functions	15
-- 5 input functions	1
-- 4 input functions	131
-- <=3 input functions	21
Dedicated logic registers	16
I/O pins	36
Total DSP Blocks	0
Maximum fan-out node	CLOCK_50-input
Maximum fan-out	16
Total fan-out	798
Average fan-out	3.07

Logic registers - 16 cause its 16 bit counter

 Cascade Counter**CASCADE COUNTER**

```

1 module divide_50000(clkin,enable,N,tick);
2
3     parameter N_BIT = 16;
4
5     input clkin;
6     input enable;
7     input [N_BIT-1:0] N;
8
9     output tick;
10
11
12     reg [N_BIT-1:0] count;
13     reg tick;
14
15     initial tick = 1'b0;
16
17     always @ (posedge clkin)
18     if (enable == 1'b1)
19     if (count == 0) begin
20         tick <= 1'b1;
21         count <= N;
22     end
23     else begin
24         tick <= 1'b0;
25         count <= count - 1'b1;
26     end
27
28 endmodule
29

```

Counts down from 49999 to 0 using clock and then creates tick then repeats so that time period of tick is 50000000/50000=1ms.

```

1 module cascade_2_top (KEY,CLOCK_50, HEX0,HEX1,HEX2,HEX3,HEX4);
2
3     input [1:0] KEY;
4     input CLOCK_50;
5     output [6:0] HEX0,HEX1,HEX2,HEX3,HEX4;|
6
7     wire [15:0] count;
8     wire [3:0] BCD0,BCD1,BCD2,BCD3,BCD4;
9     wire tick;
10    wire out_and;
11    and AND1 (out_and,!KEY[0],tick);
12
13    counter_16 count16 (CLOCK_50,out_and,count,!KEY[1]);
14    bin2bcd_16 binary_BCD_convert (count,BCD0,BCD1,BCD2,BCD3,BCD4);
15    divide50000 divide50000 (CLOCK_50,1,49999,tick);
16
17    hex_to_7seg SEG0(HEX0,BCD0);
18    hex_to_7seg SEG1(HEX1,BCD1);
19    hex_to_7seg SEG2(HEX2,BCD2);
20    hex_to_7seg SEG3(HEX3,BCD3);
21    hex_to_7seg SEG4(HEX4,BCD4);
22
23 endmodule
24

```

Experiment 7:

Original code from lecture

```

module lfsr4 (data_out, clk);
    output [4:1] data_out; // four bit random output
    input clk; // clock input

    reg [4:1] sreg; // 4 stage D-FF for this shift register
    initial sreg = 4'b1;

    always @ (posedge clk)
        sreg <= {sreg[3:1], sreg[4] ^ sreg[3]};

    assign data_out = sreg;
endmodule

```

Manually working out the first 10 sequence values

Q6	Q5	Q4	Q3	Q2	Q1	Q0	Count
0	0	0	0	0	0	1	1
0	0	0	0	0	1	1	3
0	0	0	0	1	1	1	7
0	0	0	1	1	1	1	15
0	0	1	1	1	1	1	31
0	1	1	1	1	1	1	63
1	1	1	1	1	1	1	127
1	1	1	1	1	1	0	126
1	1	1	1	1	0	1	125
1	1	1	1	0	1	0	122

XOR Q0 and Q6

LFSR modified to work for x^7

```

module LFSR_7 (
    enable,
    random_count,
    reset);
    input enable,reset;

    output [6:0] random_count;

    reg [6:0] sreg;
    initial sreg = 1'b1;


    always @ (posedge enable) begin
        if (reset==1'b1) begin
            sreg<=1'b1;
        end
        else
            sreg <= {sreg[5:0],sreg[0]^sreg[6]};
        end
        assign random_count = sreg;
    endmodule

```

Here we simply changed which registers to concatenate (we want $1+x+x^7$ so we need 0, and 6 in this system as we are starting counting from 0 not 1). To add reset functionality simply add `if(reset== 1)` inside the always block. This resetting is synchronous. Enable is set to `~KEY[3]` in the top level function, as per specification.

Test yourself task - Cascade counter

Specification diagram:

 

From this we create the top level module:

```

module casc_count_top(KEY,CLOCK_50,HEX0,HEX1,HEX2,HEX3,HEX4);

    input [1:0] KEY;
    wire [3:0] BCD0,BCD1,BCD2,BCD3,BCD4;
    input CLOCK_50;
    output [6:0] HEX0,HEX1,HEX2,HEX3,HEX4;
    wire [15:0] counter;
    wire clock_out;
    reg result;

    clkdiv temp7(CLOCK_50,clock_out);

    always @ (*)
    begin
        result <= ~KEY[0] & clock_out;
    end

    counter_16 temp0(CLOCK_50,result,~KEY[1],counter);
    bin2bcd_16 temp1(counter,BCD0,BCD1,BCD2,BCD3,BCD4);

    hex_to_7seg temp2(HEX0,BCD0);
    hex_to_7seg temp3(HEX1,BCD1);
    hex_to_7seg temp4(HEX2,BCD2);
    hex_to_7seg temp5(HEX3,BCD3);
    hex_to_7seg temp6(HEX4,BCD4);

endmodule

```

To make the divide by 50,000 tick we make a clkdiv module:

```

module clkdiv(clock_in,clock_out);

    input clock_in; // input clock on FPGA
    output reg clock_out; // output clock after dividing the input clock by divisor
    reg[15:0] counter=16'd0;
    parameter HIGH = 16'd49999;

    always @(posedge clock_in)
        begin
            if(counter == HIGH)
                begin
                    counter <= 0;
                    clock_out <= 1'b1;

                end
            else
                begin
                    counter <= counter + 1;
                    clock_out <= 1'b0;

                end
            end
        end
endmodule

```

This is developed from the one given in lecture, except with the parameter changed so that it counts to 49,999 before giving a short pulse of one, and then repeating the process.


Optional - Experiment 8

1. The circuit is triggered (or started) by pressing KEY[3] (don't forget KEY[3] is low active);
2. The 10 LEDs (below the 7-segment displays) will then start lighting up from left to right at 0.5 second interval, until all LEDs are ON;
3. The circuit then waits for a random period of time between 0.25 and 16 seconds before all LEDs turn OFF;
4. You should also display the random delay period in milliseconds on five 7-segment displays.

```

Processing  Tools  Window  Help
delay.v  lsfr14.v  fsm.v*  clktick.v  ex8_top.v*
1 module ex8_top(
2     CLOCK_50,
3     KEY,
4     HEX0,HEX1,HEX2,HEX3,HEX4,
5     LEDR);
6
7     input CLOCK_50;
8     input [3:0] KEY;
9     output [6:0] HEX0,HEX1,HEX2,HEX3,HEX4;
10    output [9:0] LEDR;
11
12    wire tick_ms;
13    wire tick_hs;
14    wire [13:0] prbs;
15    wire [3:0] BCD0,BCD1,BCD2,BCD3,BCD4;
16    wire trigger_delay;
17    wire time_out;
18    wire en_lfsr;
19    wire [15:0] counter;
20
21    clktick t0(16'd49999,1'b1,CLOCK_50,tick_ms);
22    clktick t1(16'd499,tick_ms,CLOCK_50,tick_hs);
23
24    fsm fsm_machine(tick_ms,tick_hs,~KEY[3],time_out,en_lfsr,trigger_delay,LEDR);
25    lfsr14 lsfr_part (prbs,tick_ms,en_lfsr);
26    delay delay_part(prbs,tick_ms,trigger_delay,time_out);
27
28    bin2bcd16 bin2bcd_part({2'b0,prbs[13:0]},BCD0,BCD1,BCD2,BCD3,BCD4);
29
30    hex_to_7seg SEG0(HEX0,BCD0);
31    hex_to_7seg SEG1(HEX1,BCD1);
32    hex_to_7seg SEG2(HEX2,BCD2);
33    hex_to_7seg SEG3(HEX3,BCD3);
34    hex_to_7seg SEG4(HEX4,BCD4);
35
36    endmodule
37
nming
imer)


```

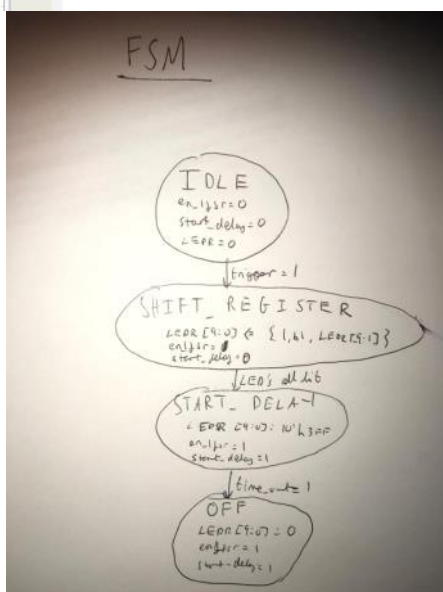

```

1 module fsm (clk,
2   tick,
3   trigger,
4   time_out,
5   en_lfsr,
6   start_delay,
7   start_reaction,
8   LEDR);
9
10  input clk,tick,trigger,time_out;
11  output en_lfsr, start_delay;
12  output [9:0] LEDR;
13
14  reg [1:0] state;
15  reg [9:0] LEDR;
16  reg en_lfsr,start_delay;
17
18  parameter IDLE = 2'b00;
19  parameter SHIFT_REGISTER = 2'b01;
20  parameter START_DELAY = 2'b10;
21  parameter OFF = 2'b11;
22
23  initial state = IDLE;
24  initial LEDR = 0;
25
26  always @(posedge clk)
27  case(state)
28
29    IDLE : if(trigger == 1'b1)
30      begin
31        state <= SHIFT_REGISTER;
32        LEDR[9:0] <= 10'h000;
33      end
34
35    SHIFT_REGISTER : if(tick == 1'b1)
36      begin
37        if(LEDR[9:0] == 10'h3FF)
38          state <= START_DELAY;
39        else
40          begin
41            LEDR[9:0] <= {1'b1,LEDR[9:1]};
42          end
43      end
44
45    START_DELAY : if(time_out == 1'b1)
46      begin
47        state <= OFF;
48        LEDR[9:0] <= 10'h000;
49      end
50
51    default : ;
52  endcase
53
54  always @ (*)
55  case(state)
56
57    IDLE :
58      begin
59        en_lfsr = 1'b0;
60        start_delay = 1'b0;
61      end
62
63    SHIFT_REGISTER :
64      begin
65        en_lfsr = 1'b1;
66        start_delay = 1'b0;
67      end
68
69    START_DELAY :
70      begin
71        en_lfsr = 1'b1;
72        start_delay = 1'b1;
73      end
74
75    OFF :
76      begin
77        en_lfsr = 1'b1;
78      end
79
80    default : ;
81  endcase
82 endmodule

```

 

The diagram for delay module:

```

37  state <= START_DELAY;
38  else
39    begin
40      LEDR[9:0] <= {1'b1,LEDR[9:1]};
41      state <= SHIFT_REGISTER;
42    end
43  end
44
45  START_DELAY : if(time_out == 1'b1)
46    begin
47      state <= OFF;
48      LEDR[9:0] <= 10'h000;
49    end
50
51  default : ;
52 endcase
53
54  always @ (*)
55  case(state)
56
57    IDLE :
58      begin
59        en_lfsr = 1'b0;
60        start_delay = 1'b0;
61      end
62
63    SHIFT_REGISTER :
64      begin
65        en_lfsr = 1'b1;
66        start_delay = 1'b0;
67      end
68
69    START_DELAY :
70      begin
71        en_lfsr = 1'b1;
72        start_delay = 1'b1;
73      end
74
75    OFF :
76      begin
77        en_lfsr = 1'b1;
78      end
79
80    default : ;
81  endcase
82 endmodule

```

```

47  OFF : state <= START_DELAY;
48  LEDR[9:0] <= 10'h000;
49
50  default : ;
51 endcase
52
53  always @ (*)
54  case(state)
55
56    IDLE :
57      begin
58        en_lfsr = 1'b0;
59        start_delay = 1'b0;
60      end
61
62    SHIFT_REGISTER :
63      begin
64        en_lfsr = 1'b1;
65        start_delay = 1'b0;
66      end
67
68    START_DELAY :
69      begin
70        en_lfsr = 1'b1;
71        start_delay = 1'b1;
72      end
73
74    OFF :
75      begin
76        en_lfsr = 1'b1;
77        start_delay = 1'b1;
78      end
79
80    default : ;
81  endcase
82 endmodule

```

Quartus Prime Lite Edition - C:/Users/duckt/Documents/ex8/ex8 - ex8_top

File Edit View Project Assignments Processing Tools Window Help

Search altera.com

Project Navigator Files

- Files
 - ./mylib/add3_ge5.v
 - ./mylib/bin2bcd_16.v
 - ./mylib/hex_to_7seg.v
 - ./ex7/ex7_top.sdc
 - ex8_top.v
 - clkclick.v
 - fsm.v
 - lsfr14.v
 - delay.v

Tasks

Compilation

Task

- Compile Design
 - Analysis & Synthesis
 - Fitter (Place & Route)
 - Assembler (Generate programming)
 - Timing Analysis
 - EDA Netlist Writer
 - Edit Settings
 - Program Device (Open Programmer)

```

1 module lfsr14(data_out,clk,enable);
2
3     output [14:1] data_out;
4     input clk,enable;
5
6     reg [14:1] sreg;
7     initial sreg = 14'b1;
8
9     reg signal;
10    initial signal = 0;
11
12    always @ (posedge clk)
13    if(signal == 0)
14    begin
15        if(enable == 1'b1)
16            signal = 1'b1;
17        else
18            sreg <= {sreg[14:1],sreg[1]^sreg[6]^sreg[10]^sreg[14]};
19        end
20    assign data_out = sreg;
21 endmodule
22

```

IP Catalog

Installed IP

Project Directory

No Selection Available

Library

- Basic Functions
- DSP
- Interface Protocols
- Memory Interfaces and Controllers
- Processors and Peripherals
- University Program
- Search for Partner IP

0% 00:00:00

Quartus Prime Lite Edition - C:/Users/duckt/Documents/ex8/ex8 - ex8_top

File Edit View Project Assignments Processing Tools Window Help

Search altera.com

Project Navigator Files

- Files
 - ./mylib/add3_ge5.v
 - ./mylib/bin2bcd_16.v
 - ./mylib/hex_to_7seg.v
 - ./ex7/ex7_top.sdc
 - ex8_top.v
 - clkclick.v
 - fsm.v
 - lsfr14.v
 - delay.v

Tasks

Compilation

Task

- Compile Design
 - Analysis & Synthesis
 - Fitter (Place & Route)
 - Assembler (Generate programming)
 - Timing Analysis
 - EDA Netlist Writer
 - Edit Settings
 - Program Device (Open Programmer)

```

1 module delay(
2     n,
3     sysclk,
4     trigger,
5     time_out
6 );
7
8     parameter BIT_SZ = 14;
9
10    input sysclk,trigger;
11    input [BIT_SZ-1:0] n;
12    output time_out;
13
14    reg [BIT_SZ-1:0] count;
15    reg time_out;
16
17    reg[1:0] state;
18    parameter IDLE = 2'b00;
19    parameter COUNTING = 2'b01;
20    parameter TIME_OUT = 2'b10;
21    parameter WAIT_LOW = 2'b11;
22
23    initial state = IDLE;
24
25    always @ (posedge sysclk)
26    case(state)
27
28        IDLE: if(trigger == 1'b1)
29            begin
30                count <= n - 1'b1;
31                state <= COUNTING;
32            end
33
34        COUNTING: if (count == 0)
35            begin
36                count <= n - 1'b1;
37                state <= TIME_OUT;
38            end
39        else
40            count <= count - 1'b1;

```

IP Catalog

Installed IP



Project Directory

No Selection Available

Library

- Basic Functions
- DSP
- Interface Protocols
- Memory Interfaces and Controllers
- Processors and Peripherals
- University Program
- Search for Partner IP

0% 00:00:00

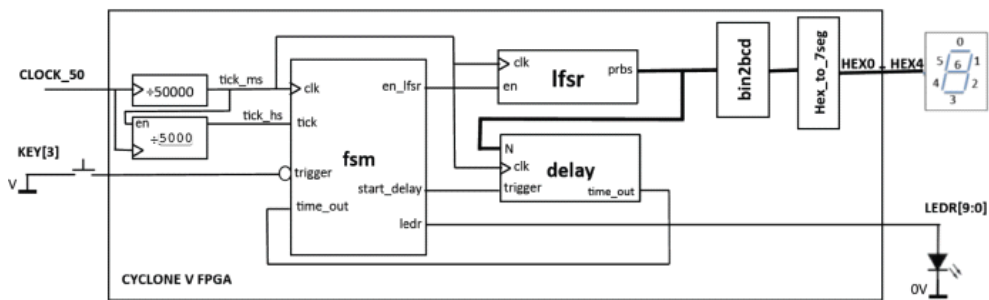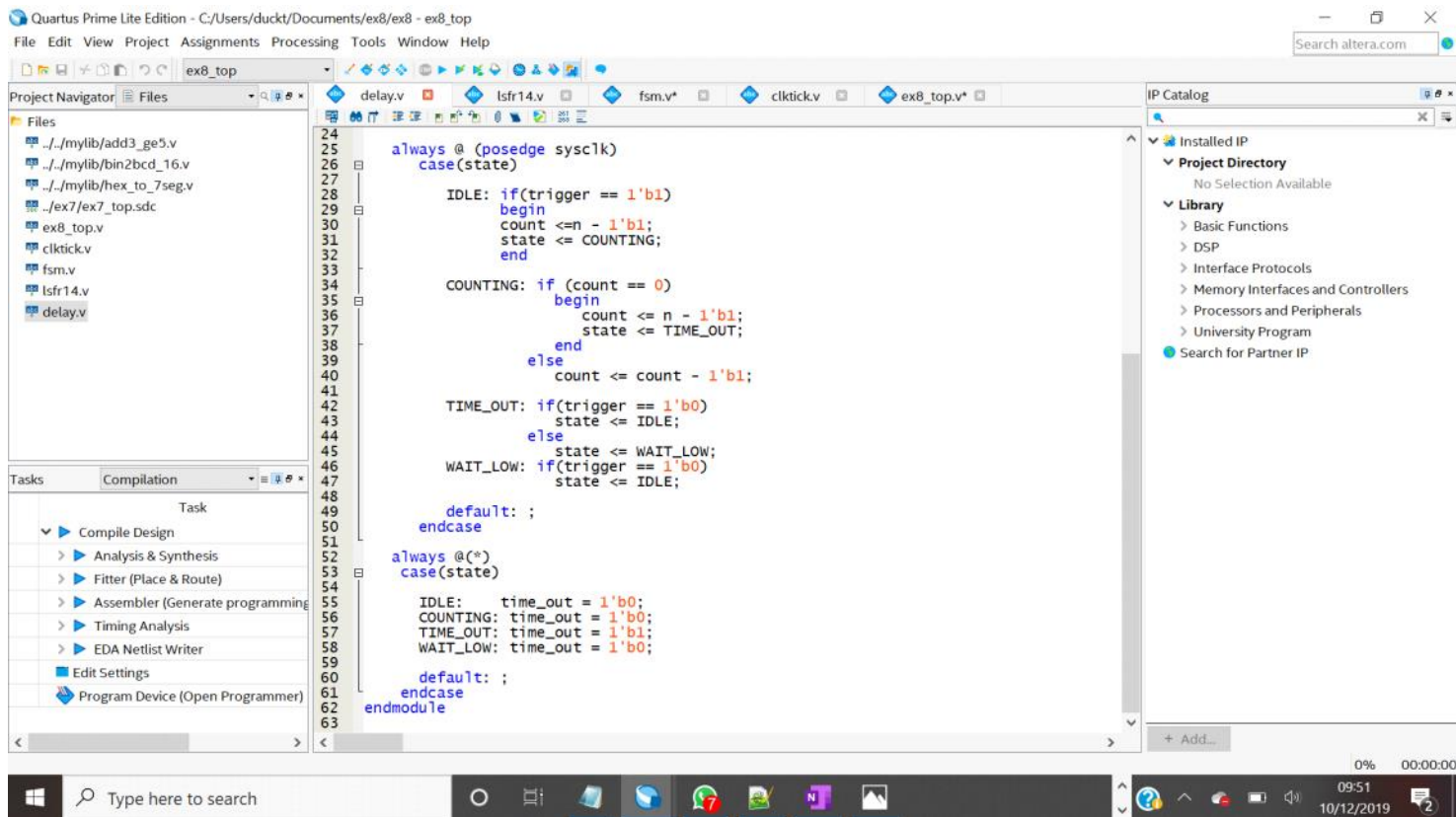

Top level module:

```

1  module ex8_top (CLOCK_50,KEY,HEX0,HEX1,HEX2,HEX3,HEX4,LEDR);
2  input CLOCK_50;
3  input [3:0] KEY;
4  output [8:0] HEX0,HEX1,HEX2,HEX3,HEX4;
5  output [9:0] LEDR;
6  wire tick_ms,tick_hs,en_lfsr,start_delay,time_out;
7  wire [7:0] bcd0,bcd1,bcd2,bcd3,bcd4;
8  wire [7:0] prbs;
9
10
11  divide divide50000 (CLOCK_50,1,16'd49999,tick_ms);
12  divide divide2500 (CLOCK_50,tick_ms,16'd2499,tick_hs);
13  fsm FSTATE_MACHINE (tick_ms,tick_hs,KEY[3],en_lfsr,start_delay,LEDR,time_out);
14
15  LFSR_8 generate_num (tick_ms,prbs,en_lfsr);
16  delay DELAY_RANDOM (tick_ms,start_delay,prbs,time_out);
17  bin2bcd_16 CONVERTER ([8'b00000000,prbs],bcd0,bcd1,bcd2,bcd3,bcd4);
18  hex_to_7seg SEG0 (HEX0,bcd0);
19  hex_to_7seg SEG1 (HEX1,bcd1);
20  hex_to_7seg SEG2 (HEX2,bcd2);
21  hex_to_7seg SEG3 (HEX3,bcd3);
22  hex_to_7seg SEG4 (HEX4,bcd4);
23
24  endmodule

```

We create one divide clock module, that takes in a number as parameter to count up to. This way we could reuse the module rather than make two for the different clocks. The top level is wired up to follow the following schematic:
The converter takes in a 16 bit number, but prbs is only 8 bits so had to be concatenated to make the correct size.

FSM module:

```

1 module fsm (clk, tick, trigger, en_lfsr, start_delay, LEDR, time_out);
2
3   input clk;
4   input tick;
5   input trigger;
6   input time_out;
7
8   reg [1:0] state;
9   parameter IDLE=0;
10
11   output en_lfsr;
12   reg en_lfsr;
13
14   output start_delay;
15   reg start_delay;
16
17   output [0:0] LEDR;
18   reg [0:0] LEDR;
19
20   //initial en_lfsr = 1;
21   initial state = IDLE;
22
23   always @ (posedge clk)
24   begin
25     if (trigger == 1 && state == IDLE)
26     state <= 1;
27     else if (time_out == 1)
28     state <= IDLE;
29
30     if (tick == 1'b1)
31     begin
32       case (state)
33       0: state <= 2;
34       1: state <= 3;
35       2: state <= 4;
36       3: state <= 5;
37       4: state <= 6;
38       5: state <= 7;
39       6: state <= 8;
40       7: state <= 9;
41       8: state <= 10;
42       9: state <= 10;
43       10: state <= 10;
44       default: ;
45     endcase
46   end
47
48   end
49
50   always @ (*)
51   begin
52     case (state)
53     IDLE:
54     begin
55       LEDR = 0;
56       en_lfsr = 1;
57       start_delay = 0;
58     end
59     1:
60     begin
61       LEDR = 1;
62       en_lfsr = 0;
63     end
64     2: LEDR = 3;
65     3: LEDR = 7;
66     4: LEDR = 15;
67     5: LEDR = 31;
68     6: LEDR = 63;
69     7: LEDR = 127;
70     8: LEDR = 255;
71     9: LEDR = 511;
72     10:
73     begin
74       LEDR = 1023;
75       start_delay = 1;
76     end
77     default: LEDR = 0;
78   endcase
79   end
80 endmodule
81
82
83
84

```

As shown in lectures we use binary encoded states. A state 'wait' must be included when waiting for the input from KEY3. This means nothing happens as state IDLE is not in the case(state) statement, and so state is not incremented until it is set to 1 first, which only happens when trigger == 1 (the key is pressed). The LFSR is initially enabled. When the key has been pressed the counting starts, the LFSR enable is set to 0, and the LEDR set to the numbers worked out for the characteristic polynomial in experiment 7. The delay module is activated and waits for the specified time before turning all LEDs off.

Delay module:

```

1 module delay(
2   sysclk, //tick_ms sysclock input
3   trigger, //input that commences the delay function when high
4   n, //binary input that dictates how long to delay for
5   time_out // goes high for 1 sysclk after n cycles
6 );
7
8   parameter BT_SZ = 8; //max delay of 2^8 clock cycles
9
10  //define input output ports
11  input trigger, sysclk;
12  input [BT_SZ-1:0] n;
13  output time_out;
14
15  //define reg variables
16  reg [BT_SZ-1:0] count;
17  reg time_out;
18
19  //state assignment of four states
20  reg [1:0] state;
21  parameter IDLE = 2'b00, COUNTING = 2'b01;
22  parameter TIME_OUT = 2'b10, WAIT_LOW = 2'b11;
23
24  initial state = IDLE;
25  initial count = n-1'b1;
26
27  //major operation is count down
28
29  always @ (posedge sysclk)
30  begin
31    case(state)
32    IDLE: if (trigger == 1'b1)
33    state <= COUNTING;
34    COUNTING: if (count == 0) begin
35    count <= n-1'b1;
36    state <= TIME_OUT;
37    end
38    else
39    count <= count-1'b1;
40    TIME_OUT: if (trigger == 1'b0)
41    state <= IDLE;
42    else
43    state <= WAIT_LOW;
44    WAIT_LOW: if (trigger == 1'b0)
45    state <= IDLE;
46    default: ; //do nothing
47    endcase
48  end
49
50  always @ (*)
51  begin
52    case(state)
53    IDLE: time_out = 1'b0;
54    COUNTING: time_out = 1'b0;
55    TIME_OUT: time_out = 1'b1;
56    WAIT_LOW: time_out = 1'b0;
57    default: ;
58    endcase
59  end
60 endmodule

```

Delay module was given in the lectures. Here we use it and change the size to 8.

The module detects a rising edge on the trigger, and counts n clock cycles, then outputs a pulse on time_out.

Optional - Experiment 9

Following Experiment 8, we add one extra module 'timer', which counts the time it takes for the user to press KEY0.

Top level module:

```

1 module ex9_top (KEY,CLOCK_50,LEDR,HEX0,HEX1,HEX2,HEX3,HEX4);
2
3 input CLOCK_50;
4 input [3:0] KEY;
5 output [6:0] HEX0,HEX1,HEX2,HEX3,HEX4;
6 output [9:0] LEDR;
7 wire tick_ms,tick_hs,en_lfsr,start_delay,time_out;
8 wire [3:0] BCD0,BCD1,BCD2,BCD3,BCD4;
9 wire [7:0] prbs;
10 wire [15:0] reaction_time;
11
12 divide divide50000 (CLOCK_50,1,16'd49999,tick_ms);
13 divide divide2500 (CLOCK_50,tick_ms,16'd2499,tick_hs);
14
15 fsm FINITE_STATE_MACHINE (tick_ms,tick_hs,!KEY[3],en_lfsr,start_delay,LEDR,time_out);
16
17 LFSR_8 generate_num (tick_ms,prbs,en_lfsr);
18 delay DELAY_RANDOM (tick_ms,start_delay,prbs,time_out);
19
20
21 timer REACTION_TIME (KEY,time_out,tick_ms,reaction_time);
22
23
24 bin2bcd_16 CONVERTER (reaction_time,BCD0,BCD1,BCD2,BCD3,BCD4);
25 hex_to_7seg SEG0 (HEX0,BCD0);
26 hex_to_7seg SEG1 (HEX1,BCD1);
27 hex_to_7seg SEG2 (HEX2,BCD2);
28 hex_to_7seg SEG3 (HEX3,BCD3);
29 hex_to_7seg SEG4 (HEX4,BCD4);
30
31 endmodule

```

This is the same as experiment 8 but with timer module included, and that the output from this is input into the BCD converter, and onto the LEDs.

Timer module:

```

1 module timer (KEY,time_out,clock,count);
2 timescale 1ns/100ps;
3 parameter BIT_SZ = 16;
4 input clock;
5 input [3:0] KEY;
6 input time_out;
7 output [BIT_SZ-1:0] count;
8 initial count = 0;
9 reg [BIT_SZ-1:0] count;
10 reg [1:0] state;
11 initial state = START;
12
13 parameter START = 2'b00, STOP = 2'b01, COUNTING = 2'b10;
14
15 always @ (posedge clock)
16 case(state)
17 START: count <= 0;
18 COUNTING: count <= count + 1'b1;
19 STOP: ;
20 endcase
21
22
23
24
25 always @ (posedge clock)
26 case(state)
27 STOP:
28 if(time_out==1)
29 state <= START;
30
31 START:
32 state <= COUNTING;
33
34 COUNTING:
35 if (KEY[0] == 0)
36 state <= STOP;
37 else
38 state <= COUNTING;
39
40 default: state <= COUNTING;
41 endcase
42
43 endmodule

```

We use one hot encoding to define the states. START sets count to 0, COUNTING increments count, and STOP does no operation. If the state is in START, then it is updated to counting, if the state is in COUNTING and the key pressed, then state is updated to STOP, otherwise it continues counting. If the state is in STOP then the state only changes to START if time_out pulse has been sent.


Operation order: time_out pulse -> state = start, LEDs display count = 0 -> state=count, LEDs display count -> key pressed-> state = STOP -> LEDs display (final) count.

Part 3

06 December 2019 20:09


Experiment 10

Schematic of Analogue I/O card:

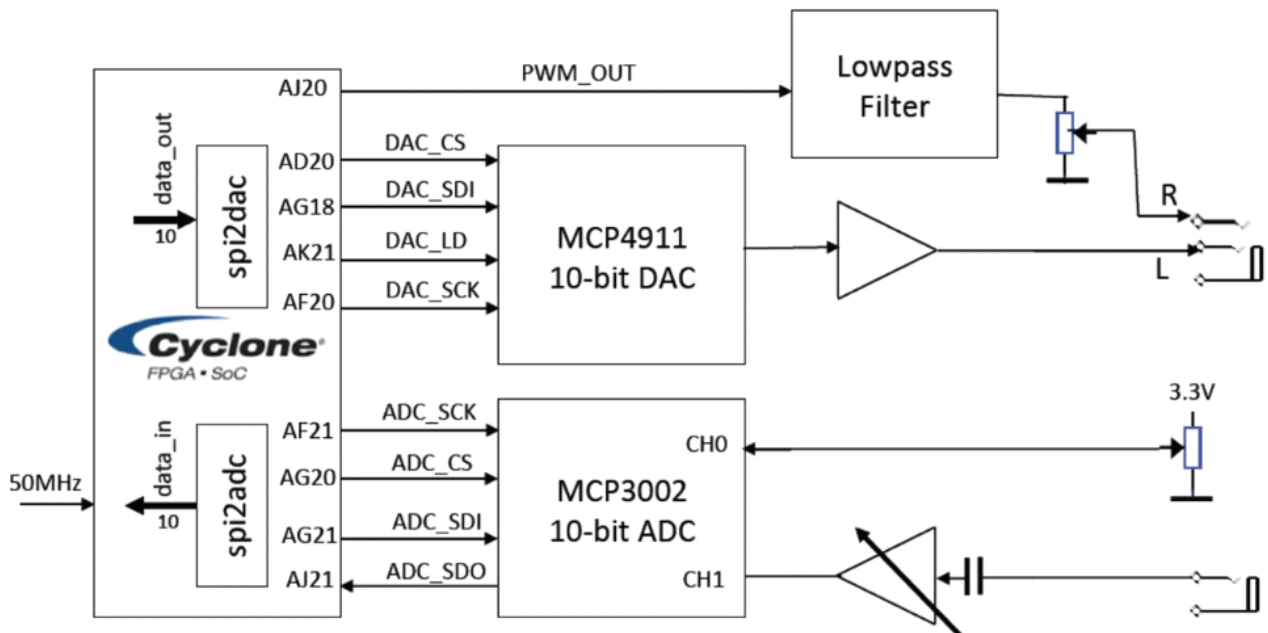

Screen clipping taken: 09/12/2019 13:24

Spi2dac code:

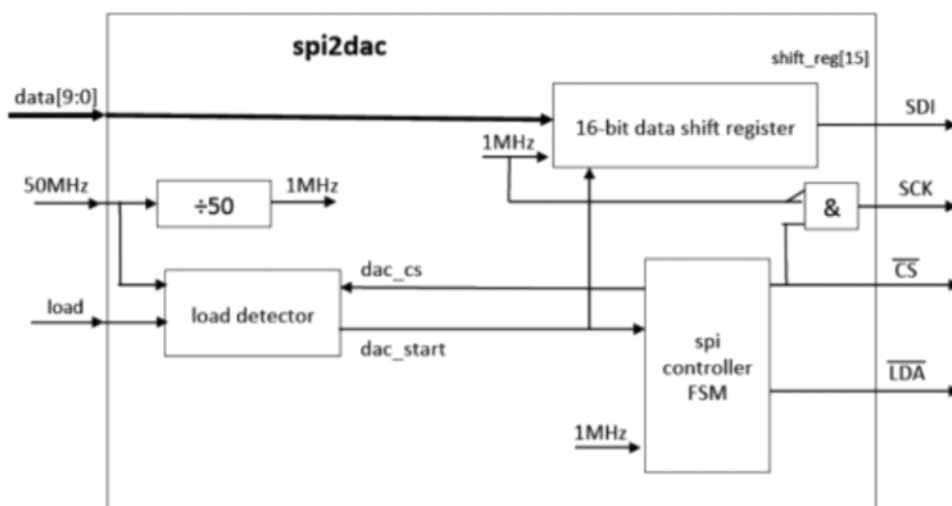

Screen clipping taken: 04/12/2019 17:28

Spi2dac takes in 2 inputs, the 10-bit data to be converted by DAC, and a load signal which triggers the data transfer and conversion to begin.

The ÷50 module produces a 1MHz clock for the FSM.

```

always @ (posedge sysclk)
  if (ctr==0) begin
    ctr <= TC;
    clk_1MHZ <= ~clk_1MHZ
  end
  else
    ctr <= ctr - 1'b1;

```

Screen clipping taken: 04/12/2019 17:49

It does this by toggling the output after 25 cycles (TC is set to 5'd24)

Load detector produces control signals to the SPI state machine and shift register.

```

always @ (posedge sysclk) // state transition
  case (sr_state)
    IDLE: if (load==1'b1) sr_state <= WAIT_CSB_FALL;
    WAIT_CSB_FALL: if (dac_cs==1'b0) sr_state <= WAIT_CSB_HIGH;
    WAIT_CSB_HIGH: if (dac_cs==1'b1) sr_state <= IDLE;
    default: sr_state <= IDLE;
  endcase

always @ (*)
  case (sr_state)
    IDLE: dac_start = 1'b0;
    WAIT_CSB_FALL: dac_start = 1'b1;
    WAIT_CSB_HIGH: dac_start = 1'b0;
    default: dac_start = 1'b0;
  endcase

```


Screen clipping taken: 04/12/2019 18:20

At each rising edge the state of FSM is checked, and updated according to the load/DAC_CS signals. The second always block sets DAC_START to high only if FSM is waiting for falling edge

Shift register sends the control bits and 10 bit data to SDI output

Predicted waveform:

Datasheet timing diagram:

 

Screen clipping taken: 04/12/2019 20:51

So according to this we predict the following output:

| Insert drawn output here |

We write the following top level code for the diagram supplied

```

module ex10_top(SW,CLOCK_50,DAC_SDI, DAC_CS, DAC_SCK, DAC_LD);

    input [9:0] SW;
    input CLOCK_50;
    wire clock_out;
    output DAC_SDI, DAC_CS, DAC_SCK, DAC_LD;


    clk_tick_16 newclock(CLOCK_50,clock_out);
    spi2dac temp(CLOCK_50, SW, clock_out, DAC_SDI, DAC_CS, DAC_SCK, DAC_LD);

endmodule


```

This is just connecting the relevant inputs/outputs to the spi2dac.

 Waveform in Modelsim after running with do file:



Actual waveform:

 

Comparing the signals we see that the predicted signal by Modelsim and the signal seen on the oscilloscope are the same when inputting the number 10'h23b.

Experiment 11

Pwm.v module:

```

module pwm (clk, data_in, load, pwm_out);

    input          clk;          // system cl
    input [9:0]    data_in;      // input dat
    input          load;         // high puls
    output         pwm_out;      // PWM outpu

    reg [9:0]      d;            // internal
    reg [9:0]      count;        // internal
    reg            pwm_out;

    always @ (posedge clk)
        if (load == 1'b1) d <= data_in;


    initial count = 10'b0;

    always @ (posedge clk) begin
        count <= count + 1'b1;
        if (count > d)
            pwm_out <= 1'b0;
        else
            pwm_out <= 1'b1;
        end
    end

```

Screen clipping taken: 04/12/2019 21:46

Diagram of how PWM works:

 

Screen clipping taken: 09/12/2019 16:24

PWM essentially compares: is the counter value \geq the data in value, if so go low, if not go high. Passing PWM through a lowpass filter gives an analogue output which is linearly related to data in.

Top level function:

```

module ex11_top(SW,CLOCK_50,DAC_SDI, DAC_CS, DAC_SCK, DAC_LD, PWM_OUT);

    input [9:0] SW;
    input CLOCK_50;
    output DAC_SDI, DAC_CS, DAC_SCK, DAC_LD, PWM_OUT;
    wire clock_out,pwm_out;


    clktick_16 temp1(CLOCK_50,clock_out);
    spi2dac temp2(CLOCK_50,SW,clock_out,DAC_SDI, DAC_CS, DAC_SCK, DAC_LD);
    pwm temp3(CLOCK_50,SW,clock_out,PWM_OUT);

endmodule

```

Again, the top level function is just connecting input/outputs to the pwm and spi2dac.

 Comparing the TP8 and TP9 values - the value is the same so we see there is no difference between using PWM or DAC.



For Pulse width modulation, the larger the input value the greater the it will be at logic high. Theoretically when all the Switches are 1, the pwm_out signal should be high all of the time, and depending upon the input, the RMS voltage will vary in proportion to the value of data_in applied. The other four outputs coming from the spi2dac module won't change.

There is a low pass filter on the add-on card, and the output seen is a flat line, retaining all the DC components but removing the high frequency components (hence why no variation in time at TP9).

Experiment 12

Used the interface to create the ROM.

Top level module:

```

module ex12_top(SW,HEX0,HEX1,HEX2,CLOCK_50);

    input [9:0] SW;
    input CLOCK_50;
    output [6:0] HEX0,HEX1,HEX2;
    wire [9:0] q;

    ROM ROMtemp(SW[9:0],CLOCK_50,q[9:0]);

    hex_to_7seg SEG0(HEX0, q[3:0]);
    hex_to_7seg SEG1(HEX1, q[7:4]);
    hex_to_7seg SEG2(HEX2, q[9:8]);


endmodule

```

The ROM stores sine values, it must be offset because the DAC only accepts positive (0-1023) so we add 512.

Experiment 13

Schematic diagram for the top level

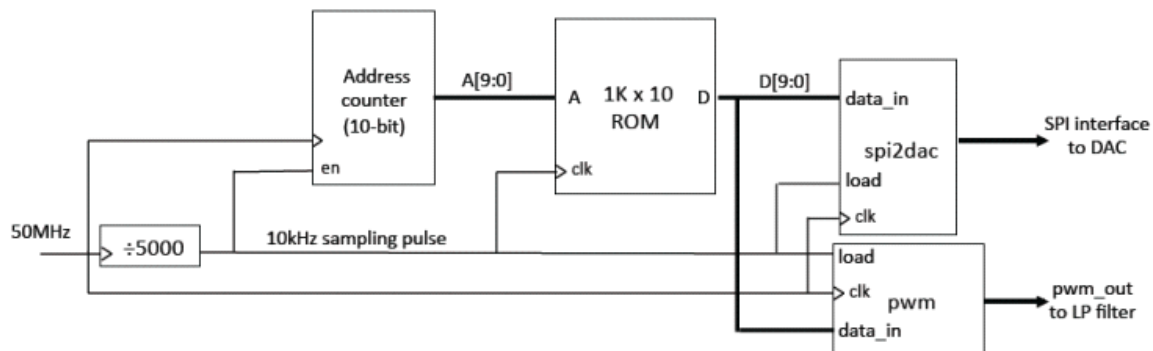

The ROM stores all the values of the sine wave as before, the counter is used to advance the phase of the sine wave (specified as the address X of ROM).

Top level module:

```

module ex13_top(CLOCK_50,DAC_CS,DAC_SDI,DAC_LD,DAC_SCK,PWM_OUT);

    input CLOCK_50;
    output DAC_CS,DAC_SDI,DAC_LD,DAC_SCK,PWM_OUT;
    wire tick;
    wire [9:0] count, out;

    clktick temp0(CLOCK_50,tick);

    counter_10 temp1(CLOCK_50,tick,count);

    ROM temp2(count,tick,out);

    spi2dac temp3(CLOCK_50,out,tick,DAC_SDI,DAC_CS,DAC_SCK,DAC_LD);

    pwm temp4(CLOCK_50,out,tick,PWM_OUT);

endmodule


```

For this we are just connecting together modules we have already made. We also make the counter 10 bit by adjusting the BIT_SZ as before in the counter module.

The frequency of the sine wave should be:

$$f = \frac{Clock_f}{2^n \times Clock_div_f} = \frac{50 \times 10^6}{1024 \times 5000} = 9.76 \text{ Hz}$$


From the oscilloscope we measure:

 

Freq = 9.77 Hz, and amplitude 0-3.3V.

Optional - Experiment 14

Schematic diagram for the top level:

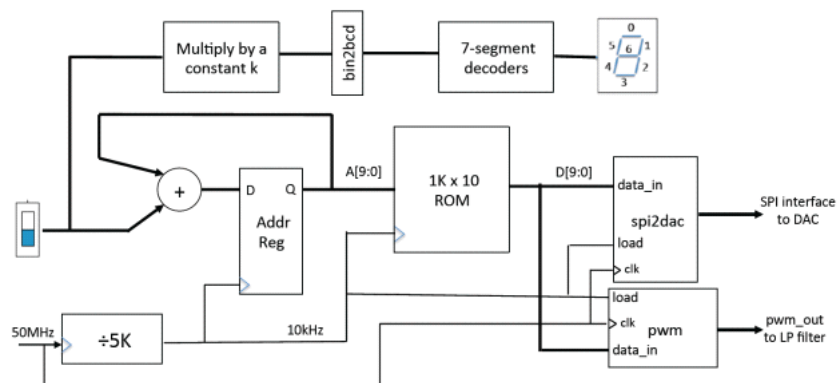

In order to get the frequency you take the top 14 bits as this is the same as dividing by 1024

Top level module:

```

module ex14_top(SW,CLOCK_50,DAC_CS,DAC_SDI,DAC_LD,DAC_SCK,PWM_OUT,HEX0,HEX1,HEX2,HEX3,HEX4);

    input [9:0] SW;
    output [6:0] HEX0,HEX1,HEX2,HEX3,HEX4;
    input CLOCK_50;
    output DAC_CS,DAC_SDI,DAC_LD,DAC_SCK,PWM_OUT;

    wire [23:0] mult;
    wire [9:0] A,D,q;
    wire clock_10;
    wire [3:0] BCD0, BCD1, BCD2, BCD3, BCD4;

    clktick temp0(CLOCK_50,clock_10);
    ROM temp1(D[9:0],clock_10,q[9:0]);
    spi2dac temp2(CLOCK_50, q[9:0], clock_10, DAC_SDI, DAC_CS, DAC_SCK, DAC_LD);
    pwm temp3(CLOCK_50, q[9:0], clock_10, PWM_OUT);
    bin2bcd_16 temp4({2'b0,mult[23:10]},BCD0,BCD1,BCD2,BCD3,BCD4);
    mult_temp5 (SW[9:0], 10000, mult);
    addr_reg temp6(A[9:0]+SW[9:0],D[9:0],clock_10);

    hex_to_7seg SEG0(HEX0,BCD0);
    hex_to_7seg SEG1(HEX1,BCD1);
    hex_to_7seg SEG2(HEX2,BCD2);
    hex_to_7seg SEG3(HEX3,BCD3);
    hex_to_7seg SEG4(HEX4,BCD4);

endmodule

```

Where clktick has been changed to count up to 5000 before giving a high pulse. Mult was made using the IP catalog.

Addr_reg:

```

module addr_reg(D,Q,clk);

    input [9:0] D;
    output reg [9:0] Q;
    input clk;

    always @ (posedge clk)
        begin
            Q[9:0] <= Q[9:0] + D[9:0];
        end

endmodule

```

This module simply adds the input and output of a flip flop, on a clock high.

This circuit works as following:

1. For a combination of input switches, the number is multiplied and then converted into BCD and displayed on 7-segment displays
2. This number is input to a D flip flop, and added to the current Q.
3. A 50MHz clock is divided with clktick which clocks the flip flop and ROM, and serves as the load to spi2dac and pwm.
4. The output Q is used as the address to obtain the value in ROM, which is used as the data in to the spi2dac and pwm.

Part 4

06 December 2019 20:09

Part 4

Experiment 16

If you associate the signal names inside the module to outside it allows connections to be defined independent of order.

```
spi2adc SPI_ADC (  
    .sysclk (CLOCK_50),  
    .channel (1'b1),  
    .start (tick_10k),  
    .data_from_adc (data_in),  
    .data_valid (data_valid),  
    .sdata_to_adc (ADC_SDI),  
    .adc_cs (ADC_CS),  
    .adc_sck (ADC_SCK),  
    .sdata_from_adc (ADC_SDO));
```

All pass module corrects ADC converter data by subtracting offset from data_out to get a 2's complement value x. It connects x to y, and converts y from 2's complement to offset binary for DAC.

```
1 module processor (sysclk, data_in, data_out);  
2  
3  
4 input sysclk; // system clock  
5 input [9:0] data_in; // 10-bit input data  
6 output [9:0] data_out; // 10-bit output data  
7  
8 wire sysclk;  
9 wire [9:0] data_in;  
10 reg [9:0] data_out;  
11 wire [9:0] x,y;  
12  
13 parameter ADC_OFFSET = 10'h181;  
14 parameter DAC_OFFSET = 10'h200;  
15  
16 assign x = data_in[9:0] - ADC_OFFSET; // x is input in 2's complement  
17 assign y = x+x+x+x;  
18  
19 //multiply the input by a factor of four and store the result in y  
20  
21 // Now clock y output with system clock  
22 always @(posedge sysclk)  
23 data_out <= y + DAC_OFFSET;  
24  
25 endmodule  
26
```

Mult.v can be done by shifting by 2 (assign $y = x \ll 2$), adding x 4 times to itself (as done here), or making a multiply module.

Experiment 17

Schematic:



Top level file is the same as ex 16 with the following additions:

```
pulse_gen temp(pulse, data_valid, CLOCK_50);  
processor simple_echo (CLOCK_50, data_in, data_out, pulse); // do some processing on the data
```

We create a FIFO component of size 8192 x 10 bit using the IP catalog. In FIFO received data is stored in a sequence so it can be retrieved in the order it arrived in. If data is retrieved it is removed which can cause the rates to be different. If the send is greater than retrieve rate then the buffer will get full, and should not receive more data. Empty buffers cannot provide data for retrieval. This FIFO is used to implement the delay.

Pulse generator module:

```

module pulse_gen(pulse, in, clk);

    output        pulse; // output pulse lasting one clk cycle
    input         in;     // input, +ve edge to be detected
    input         clk;    // clock signal

    reg [1:0]     state;
    reg          pulse;

    parameter     IDLE = 2'b0; // state coding for IDLE state
    parameter     IN_HIGH = 2'b01;
    parameter     WAIT_LOW = 2'b10;

    initial state = IDLE;

    always @ (posedge clk)
    begin
        pulse <= 0; // default output
        case (state)
            IDLE: if (in == 1'b1) begin
                                state <= IN_HIGH;    pulse <= 1'b1; end
                            else
                                state <= IDLE;

            IN_HIGH: if (in == 1'b1)
                                state <= WAIT_LOW;
                            else
                                state <= IDLE;

            WAIT_LOW: if (in == 1'b1)
                                state <= WAIT_LOW;
                            else
                                state <= IDLE;

            default: ;
        endcase
    end //... always
endmodule

```

This sets the state to IDLE, unless in == 1, in which case it only sets pulse to 1 if the current state is IDLE, in all other states they are set to WAIT_LOW.

Processor module changes:

```

wire          full;
wire [9:0]    q;
reg           DFF;
wire          data_valid;

initial       DFF = 0;

fifo          delay(sysclk, x , (DFF&wrreq), wrreq, full, q[9:0]);

assign       y = {q[9],q[9:1]} + x[9:0];


```

The FIFO is used to create a delay. The concatenation is effectively divide by 2 (it removes LSB, and extends by MSB) which implements the attenuation required. We also set the DFF <= full in the always block after this.

Experiment 18

The only change to this needed is to take away the output of the FIFO rather than add in the echo module. No other changes were made anywhere.

Schematic diagram:

 

Changes in echo module:

```

assign       y = x[9:0] - {q[9],q[9:1]};

```

Experiment 19

Top level module changes:


```

processor variable_delay(CLOCK_50, data_in, data_out, data_valid,Sw, BCD_0, BCD_1, BCD_2);

```

Variable delay:

Schematic:

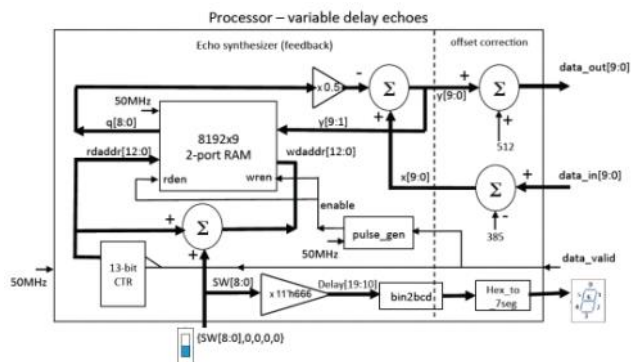

Changes to processor:

```

assign          wdaadr = rdaadr + {SW[8:0],4'b0};
assign          Delay = SW[8:0] * 11'h666;
bin2bcd_16      temp({5'b0,Delay[19:10]},BCD_0, BCD_1, BCD_2, BCD_3, BCD_4);
pulse_gen       temp2(pulse,data_in,sysclk);
wire            data_valid;

counter_13      mycount(sysclk,data_valid,rdaadr);
delay_ram       myRam(sysclk,y[9:1],rdaadr,pulse,wdaadr,pulse,q);

assign          y = x[9:0] - {q[8],q[8],q[8:2]};

```

Write address = read address + switches (concatenated with 0's to make correct size)

Delay = switches multiplied by 1638

Take the most significant bits of Delay, concatenate to make correct size for BCD converter

Counter to get read address

Ram delay

As before to attenuate

We use the catalog IP to create the RAM, with one write port (to store ADC samples) and one read port. A 13 bit counter is used to generate the read address to the RAM - we reuse the module counter, and edit BIT_SZ to 13 (this is because the RAM is 8192 x 9 bit, and $2^{13} = 8192$). The address generator computes the address used on the next read and write cycle as it is incremented on the negative edge of the data valid signal. The write address = read address + SW[8:0]. Embedded memory in FPGA is 9 bit data width not 10 bit, so read value and write value are truncated to 9 bits. To display the delay value SW[8:0] is multiplied by 1638 and a constant. The most significant 10 bits is the delay in ms. Then it is converted from binary to BCD to display on 7 segs.

Part 3me

10 December 2019 09:18

EXPERIMENT 10 - Interface with the MCP4911 Digital-to-Analogue Converter

We have a DAC_CS signal that enables the DAC when it is low...

The following test bench do file enabled the SPI2DAC module to be loaded with a data input *data_in*. In addition to a system clock that will allow the data to be read upon the rising edge of the clock and read out as analogue voltages. Once the load pulse has gone high for a period for one clock cycle, then we commence the conversion from digital to analogue. All of the pins *dac_sdi*, *dac_cs*, *dac_sck*, *dac_ld* can be recorded off the various pins on the add on card circuit.

Configuration bit settings

Bit 15 = 0 : write to DAC register

Bit 14 = 0: input buffer control bit is 0

Bit 13 = 1: 1*vout


Bit 12 = 1: shutdownbar = 1. enable operation of DAC.

```
H:/VERI/Part 3/tb_spi2dac.do - Default
Ln#
1  add wave -position end sysclk
2  add wave -position end -hexadecimal data_in
3  add wave -position end load
4  add wave -position end dac_sdi
5  add wave -position end dac_cs
6  add wave -position end dac_sck
7  add wave -position end dac_ld
8  force sysclk 1 0, 0 10ns -r 20ns
9  force data_in 10'h23b
10 force load 0
11 run 200ns
12 force load 1
13 run 400ns
14 force load 0
15 run 20us
16
```

The results we obtained from this .do file being called upon in the command line I the following:



It is important to set up the waveforms to be displayed by using various *add wave* commands for the multiple inputs (including *load* and *data_in*) and outputs (like *dac_SCK*, *data_SDI*) that we have. Once the DAC has been loaded the *dac_ld* signal will remain high whilst all of the data is being read in from the *dac_sdi* input. As specified from the code above the system clock *sysclock* is specified as a 20ns square wave clock, and simply specify the load signal to give a short lasting pulse. Whenever the *dac_ld* signal is high, we have that the system clock behaves as it is expected to.

 

The *data_in* value determined by the 10 switches (*SW[9:0]*) is loaded to the *spi2dac* module at a rate of 10k samples per second as governed by the *load* signal. The steps for this part are:

Measurements on the Oscilloscope



DAC output(TP8) with DVM when SW{9:0} =0


The main principle behind digital to analogue converter is that if we supply a larger binary input, then we will get a larger analogue voltage out and vice versa. We noticed from our readings that when changed the switch positions, the DC voltage read would change in height for different values.

Theoretically, we require that the input divided by the maximum input represent the proportion of the maximum output voltage that we can obtain. More specifically:

$$\frac{IN[9:0]}{1024} V_{out_{max}} = V_{out} \quad \text{where } V_{out_{max}} = 3.3V$$



DAC_CS

 

DAC_SDI

Part 4 me

EXPERIMENT 16

```
1 module processor (sysclk, data_in, data_out);
2
3     input sysclk; // system clock
4     input [9:0] data_in; // 10-bit input data
5     output [9:0] data_out; // 10-bit output data
6
7     wire sysclk;
8     wire [9:0] data_in;
9     reg [9:0] data_out;
10    wire [9:0] x,y;
11
12    parameter ADC_OFFSET = 10'h181;
13    parameter DAC_OFFSET = 10'h200;
14
15    assign x = data_in[9:0] - ADC_OFFSET; // x is input in 2's complement
16    assign y = x+x+x+x;
17
18    //multiply the input by a factor of four and store the result in y
19    // Now clock y output with system clock
20    always @(posedge sysclk)
21        data_out <= y + DAC_OFFSET;
22
23 endmodule
24
25
26
```

The multiply block can be done by adding the same entity four times to itself. It can also be done by simply left shifting the binary number twice. However it can also be done by creating a multiply module.

The all pass processor does not do any signal processing other than just shift by two different quantities.


EXPERIMENT 17

```
processor echo_delay (data_in,data_valid, CLOCK_50, data_out); // do some processing on the data
hex_to_7seg SEG0 (HEX0, data_in[3:0]);
hex_to_7seg SEG1 (HEX1, data_in[7:4]);
hex_to_7seg SEG2 (HEX2, {2'b0,data_in[9:8]});

endmodule
```

The above picture represents the only part that changed from the top file in experiment 16. The other parts included instantiating the DAC and ADC modules, which need not be changed for this experiment.

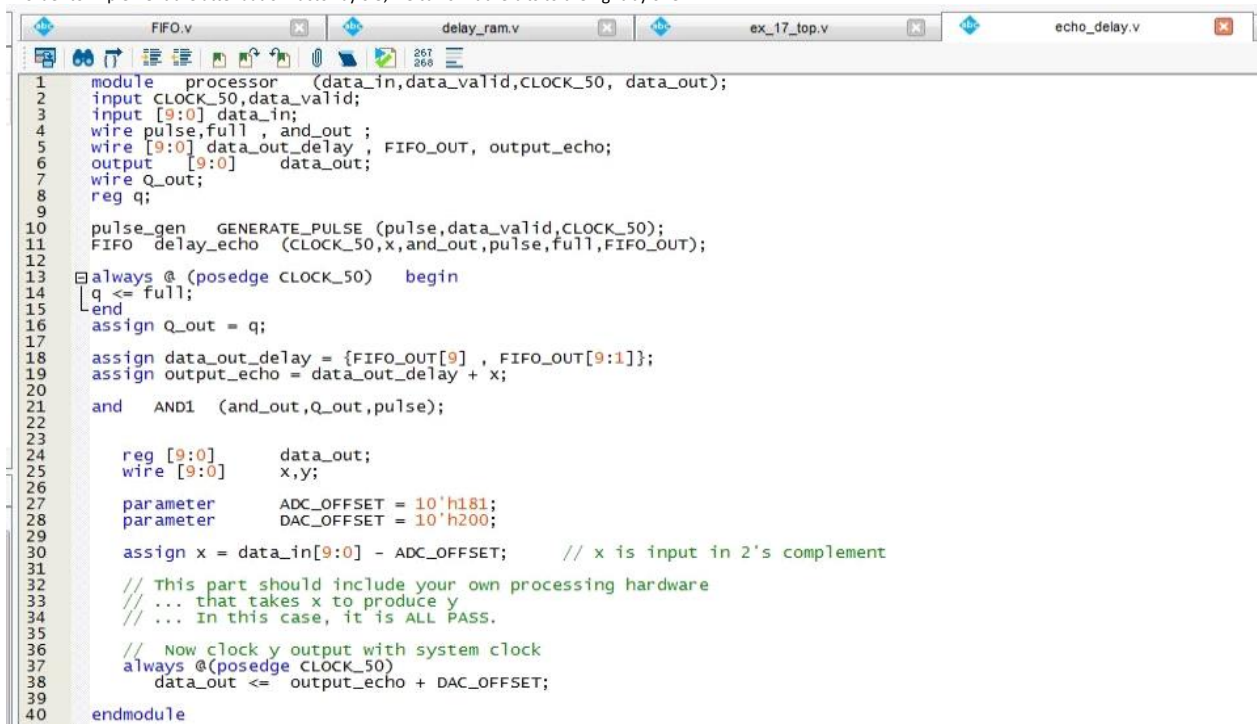In order to implement the attenuation factor by 0.5, we can shift the bits to the right by one.



```
1 module processor (data_in,data_valid,CLOCK_50, data_out);
2     input CLOCK_50,data_valid;
3     input [9:0] data_in;
4     wire pulse,full , and_out ;
5     wire [9:0] data_out_delay , FIFO_OUT, output_echo;
6     output [9:0] data_out;
7     wire Q_out;
8     reg q;
9
10    pulse_gen GENERATE_PULSE (pulse,data_valid,CLOCK_50);
11    FIFO delay_echo (CLOCK_50,x,and_out,pulse,full,FIFO_OUT);
12
13    always @ (posedge CLOCK_50) begin
14        q <= full;
15    end
16    assign Q_out = q;
17    assign data_out_delay = {FIFO_OUT[9] , FIFO_OUT[9:1]};
18    assign output_echo = data_out_delay + x;
19
20    and AND1 (and_out,Q_out,pulse);
21
22
23    reg [9:0] data_out;
24    wire [9:0] x,y;
25
26    parameter ADC_OFFSET = 10'h181;
27    parameter DAC_OFFSET = 10'h200;
28
29    assign x = data_in[9:0] - ADC_OFFSET; // x is input in 2's complement
30
31    // This part should include your own processing hardware
32    // ... that takes x to produce y
33    // ... In this case, it is ALL PASS.
34
35    // Now clock y output with system clock
36    always @(posedge CLOCK_50)
37        data_out <= output_echo + DAC_OFFSET;
38
39 endmodule
40
41
```

We use the FIFO to implement the constant delay, which we find from the IP Catalogue. We fill up the FIFO first using the write request and when it is full, we starting reading the elements from the FIFO as a stream of binary data upon every active edge of the clock.

```

1 module pulse_gen (pulse , in , clk);
2 input in,clk;
3 output pulse;
4
5 reg [1:0] state;
6 reg pulse;
7
8 //define state binary encoding
9
10 parameter IDLE = 2'b00;
11 parameter IN_HIGH = 2'b01;
12 parameter WAIT_LOW = 2'b10;
13
14 initial state = IDLE;
15 initial pulse = 1'b0;
16
17 always @ (posedge clk)
18 case (state)
19 IDLE: if (in == 1'b1) state <= IN_HIGH;
20 IN_HIGH: if (in == 1'b1) state <= WAIT_LOW;
21           else state <= IDLE;
22 WAIT_LOW: if (in == 1'b0) state <= IDLE;
23 default: ;
24 endcase
25
26 always @ (*)
27 case (state)
28 IDLE: pulse = 1'b0;
29 IN_HIGH: pulse = 1'b1;
30 WAIT_LOW: pulse = 1'b0;
31 endcase
32
33 endmodule

```

The data valid signal is applied as input to the pulse gen module, which gives a pulse lasting for one cycle once it has counted up.

In order to implement the attenuation factor by 0.5, we can shift the bits to the right by one. No adder block module is needed to implement the addition.

```

10 pulse_gen GENERATE_PULSE (pulse,data_valid,CLOCK_50);
11 FIFO delay_echo (CLOCK_50,output_echo,and_out,pulse,full,FIFO_OUT);
12
13 always @ (posedge CLOCK_50) begin
14 q <= full;
15 end
16 assign Q_out = q;
17
18 assign data_out_delay = {FIFO_OUT[9] , FIFO_OUT[9:1]};
19 assign output_echo = x-data_out_delay;
20
21 and AND1 (and_out,Q_out,pulse);
22
23
24 reg [9:0] data_out;
25 wire [9:0] x,y;
26
27 parameter ADC_OFFSET = 10'h181;
28 parameter DAC_OFFSET = 10'h200;
29
30 assign x = data_in[9:0] - ADC_OFFSET; // x is input in 2's complement
31

```

EXPERIMENT 19

```

8 module variable_echo_delay (SW,CLOCK_50,data_valid,data_in,data_out,HEX0,HEX1,HEX2,HEX3);
9
10 input CLOCK_50; // DE0 50MHZ system clock
11 input [9:0] data_in;
12 output [9:0] data_out;
13 input data_valid;
14 input [8:0] SW; // 10 slide switches to specify address to ROM
15 output [6:0] HEX0, HEX1, HEX2,HEX3;
16
17 wire [12:0] count_out,add_out;
18 wire [9:0] x; // converted data from ADC
19 // processed data to DAC
20 wire data_valid , enable;
21 wire DAC_SCK, ADC_SCK;
22 wire [9:0] y;
23 wire [8:0] q , q_divide_2;
24 wire [19:0] Delay;
25 wire [3:0] BCD0,BCD1,BCD2,BCD3;
26 parameter ADC_OFFSET = 10'h181;
27 parameter DAC_OFFSET = 10'h200;
28 counter_13 NEG_EDGE_COUNTER (data_valid, 1,count_out,0);
29
30 assign add_out = {SW[8:0],4'b0000} + count_out; // check the sw
31
32 RAM_2_port DELAY_BLOCK (CLOCK_50,y[9:1],count_out,enable, add_out, enable , q);
33 multiplier MULT (SW[8:0],Delay);
34 bin2bcd10 CONVERTER (Delay[19:10],BCD0,BCD1,BCD2,BCD3);
35 pulse_gen PULSE_GENERATOR (enable,data_valid,CLOCK_50);
36
37 hex_to_7seg SEG0 (HEX0,BCD0);
38 hex_to_7seg SEG1 (HEX1,BCD1);
39 hex_to_7seg SEG2 (HEX2,BCD2);
40 hex_to_7seg SEG3 (HEX3,BCD3);
41
42 assign q_divide_2 = {q[8],q[8:1]};
43
44 assign x = data_in - ADC_OFFSET;
45 assign y = x - q_divide_2;
46
47
48 assign data_out = y + DAC_OFFSET;
49
50 endmodule
51
52

```

variable_echo_delay PROCESSOR (SW,CLOCK_50,data_valid,data_in,data_out,HEX0,HEX1,HEX2,HEX3); // do some processing on the data

All of the other code stayed the same. We used channel one for the analogue input. Only the signal processing is changed. ex